

Read-Only Memory


ROM

ROM

- **Can be used:**
 - to implement any arbitrary combinational circuit
 - as a memory
- **Consists of:**
 - an n -to- 2^n decoder that produces ALL minterms
 - a set of programmable OR gates that produce SoP's
- **Is usually described in terms of:**
 - size of its decoder output (number of memory rows)
 - number of OR gates (memory width)
 - i.e., $2^n \times w$, e.g., 8×4 , 1024×8 , etc.


ROM: Example 1

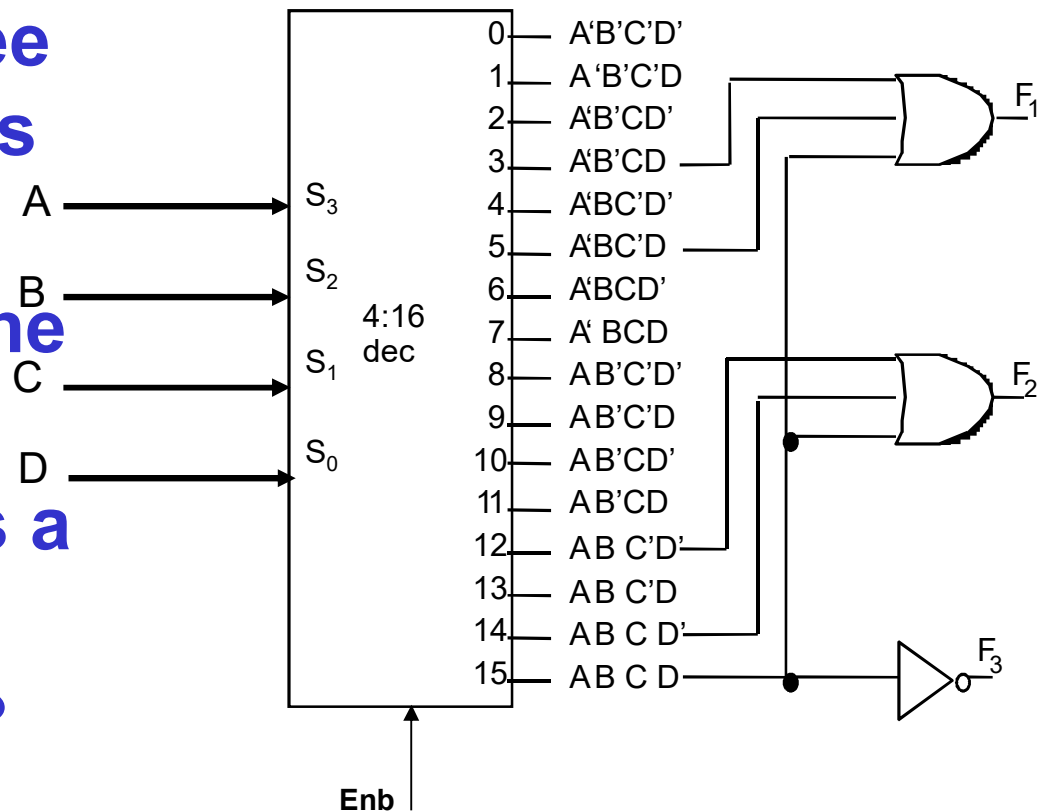- A 4-to-16 decoder
- Three OR gates
- Implemented three Boolean functions
- Has an “enable” input to control the output
- Can be viewed as a 16 x 3 memory
- Memory content?




ROM: Example 2

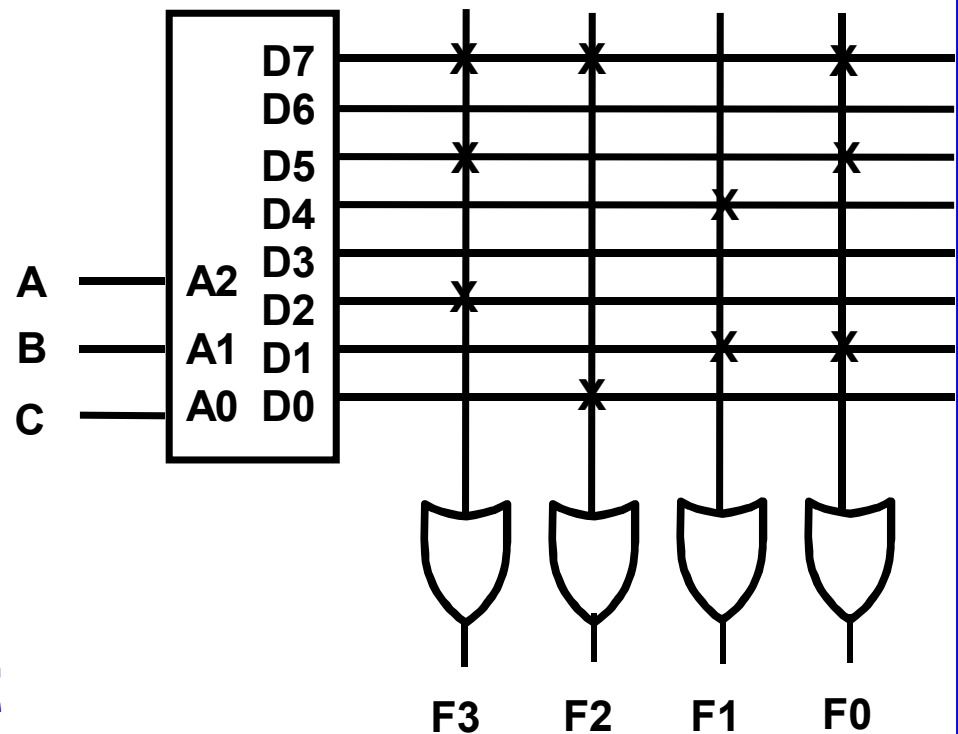
- A 3-to-8 decoder
- Four OR gates
- Can implement four Boolean functions
- Can be viewed as a 8 x 4 memory
- No “enable” input
- Memory content?




ROM vs. PLA/PAL

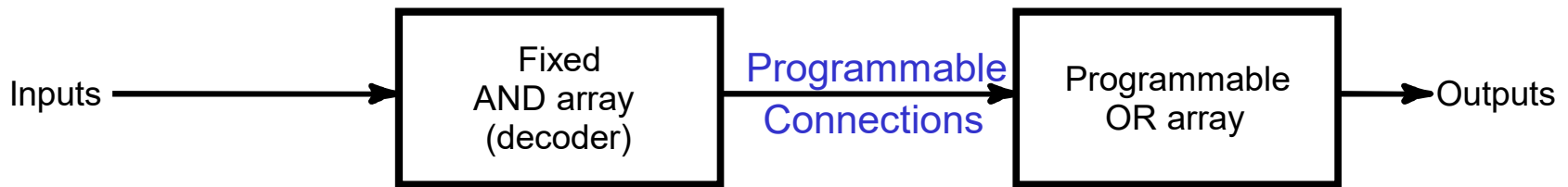

(a) Programmable read-only memory (PROM)

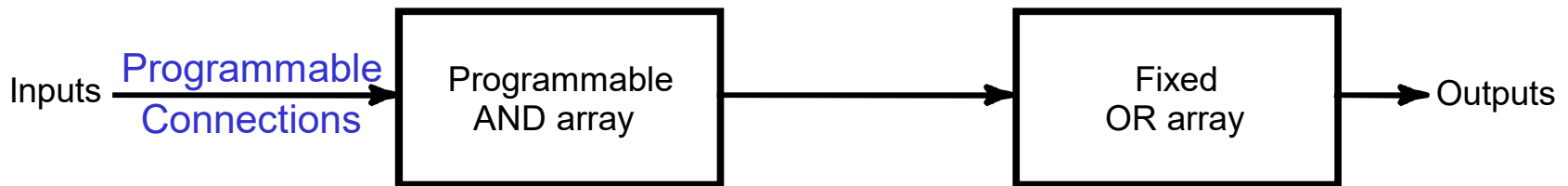

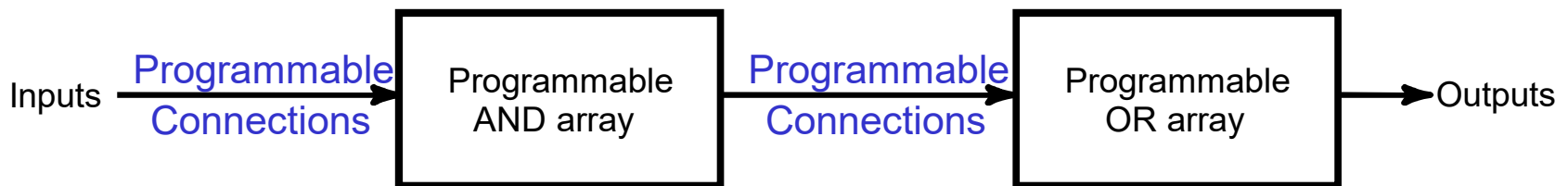(b) Programmable array logic (PAL) device




(c) Programmable logic array (PLA) device

ROM as a Memory

- ROM's can be viewed as memory with the inputs as address lines, and outputs as the stored data
- Usually have:
 - N input lines,
 - M output lines,
 - Provide $2^N \times M$ bits of memory

ROM as Memory (Example)

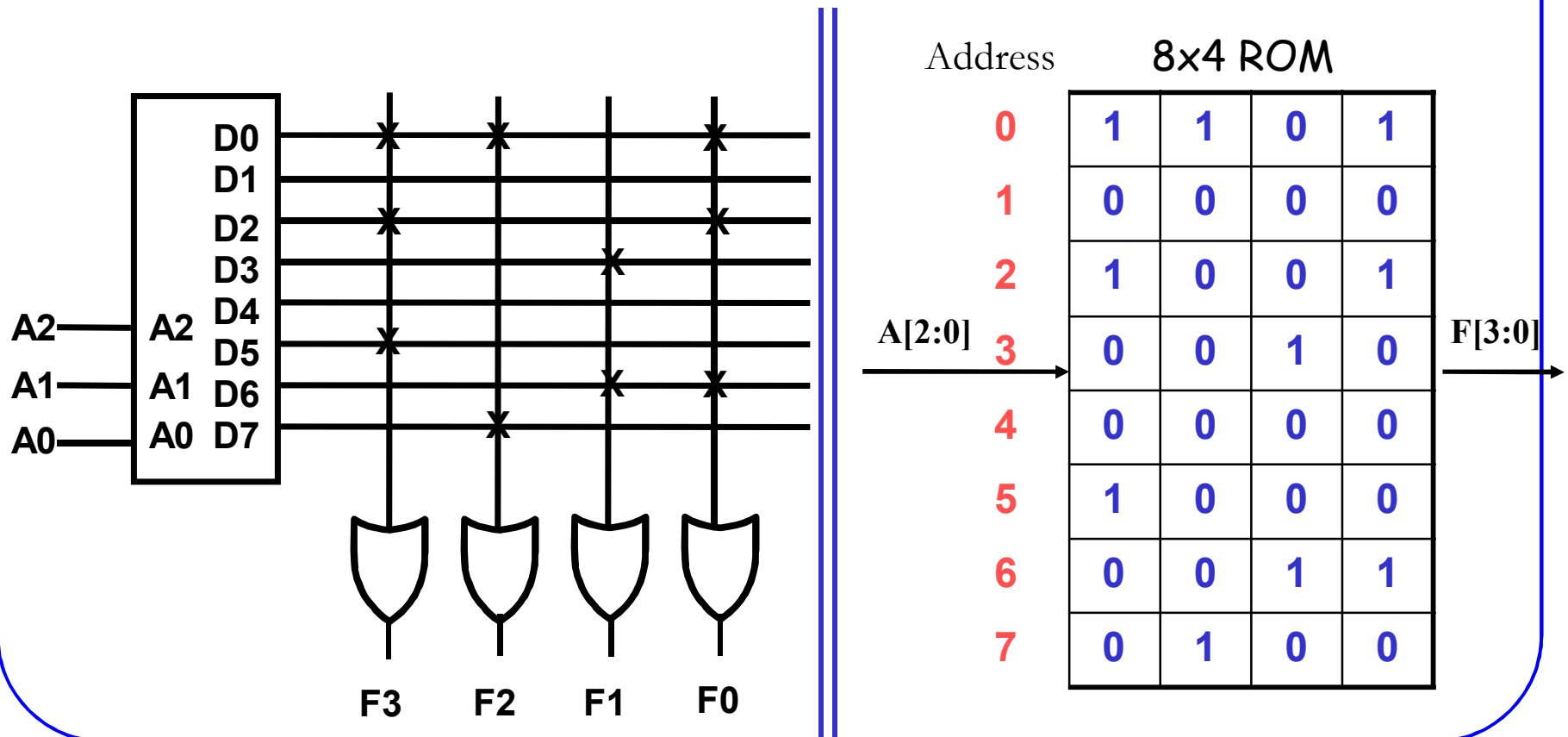- **Read Example:** For input $(A_2, A_1, A_0) = 011$, output is $(F_3, F_2, F_1, F_0) = 0010$.
- What are functions F_3, F_2, F_1 and F_0 in terms of (A_2, A_1, A_0) ?



(Memories)

- **Volatile:**

- Random Access Memory (RAM):
 - SRAM: "static"
 - DRAM: "dynamic"

- **Non-Volatile:**

- ROM
- PROM
- EPROM
- EEPROM
- FLASH memory: similar to EEPROM with programmer integrated on chip