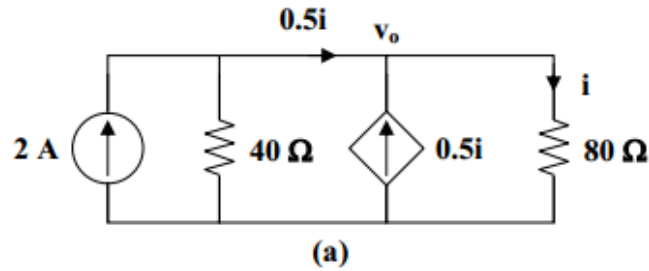


## جواب تمرینات سری چهارم

-۲

Before  $t = 0$ , the circuit has reached steady state so that the capacitor acts like an open circuit. The circuit is equivalent to that shown in Fig. (a) after transforming the voltage source.




$$0.5i = 2 - \frac{v_o}{40}, \quad i = \frac{v_o}{80}$$

$$\text{Hence, } \frac{1}{2} \frac{v_o}{80} = 2 - \frac{v_o}{40} \longrightarrow v_o = \frac{320}{5} = 64$$


$$i = \frac{v_o}{80} = \underline{\underline{0.8 \text{ A}}}$$

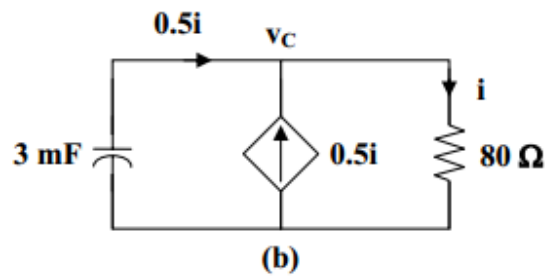After  $t = 0$ , the circuit is as shown in Fig. (b).



$$v_C(t) = v_C(0)e^{-t/\tau}, \quad \tau = R_{th}C$$

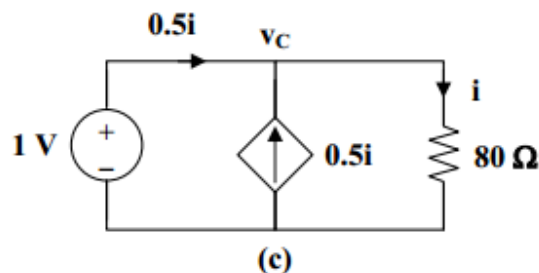To find  $R_{th}$ , we replace the capacitor with a 1-V voltage source as shown in Fig. (c).



$$i = \frac{v_c}{80} = \frac{1}{80}, \quad i_o = 0.5i = \frac{0.5}{80}$$


$$R_{th} = \frac{1}{i_o} = \frac{80}{0.5} = 160 \, \Omega, \quad \tau = R_{th}C = 480$$

$$v_c(0) = 64 \, V$$

$$v_c(t) = 64 e^{-t/480}$$

$$0.5i = -i_c = -C \frac{dv_c}{dt} = -3 \left( \frac{1}{480} \right) 64 e^{-t/480}$$
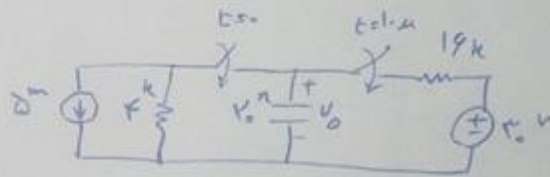
$$i(t) = \underline{0.8 e^{-t/480} \, u(t) A}$$



چون شارژ دارای ولتاژ اولیه نیست  
همچنین در لحظه وقوع ولتاژ خروجی  
خاموشی در ولتاژ خروجی است.

۳) برای حل این نوع سوالات به چند  
حالت کلیدزنی داریم باید مواظب باشیم  
از ای زمانهای مختلف حل کرد.

در  $0 < t < 1\text{ms}$



$$V_o(\infty) = -4 \times 5 = -20\text{V}$$

پس مدار  $V_o$  در بازه  $0 < t < 1\text{ms}$  به صورت زیر است:


$$\tau = R_{eq}C = 4 \times 10^{-3} = 4\text{ms}$$

$$V_o = V_o(\infty) + (V_o(0) - V_o(\infty))e^{-\frac{t}{\tau}}$$

$$V_o = -20 + (0 - (-20))e^{-\frac{t}{4\text{ms}}}$$

$$V_o = -20(1 - e^{-12500t}) \quad 0 < t < 1\text{ms}$$

در  $1\text{ms} < t < \infty$

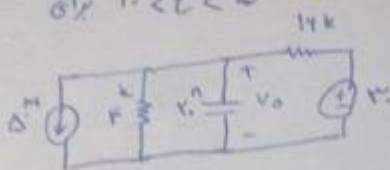


چون ولتاژ خروجی تغییراتی ندارد پس ولتاژ شارژ در  $V_o(1\text{ms})$

برابر است با ولتاژ شارژ در  $V_o(1\text{ms})$  پس داریم:

$$V_o(1\text{ms}) = -20(1 - e^{-12500 \times 1\text{ms}}) = -2.35$$

$$V_o(\infty) = ?$$

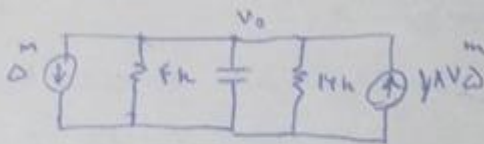

$$R_{eq} = 19 \parallel 2 = 1.7\text{k}$$

$$I_{eq} = 5 - 11.125 = 3.125\text{mA}$$




$$V_o(\infty) = 3.125 \times 19 = -10$$

$$\tau = R_{eq}C = 1.7 \times 10^{-3} = 1.7\text{ms}$$

$$V_o(t) = -10 + (-2.35 + 10)e^{-\frac{(t-1\text{ms})}{1.7\text{ms}}}$$
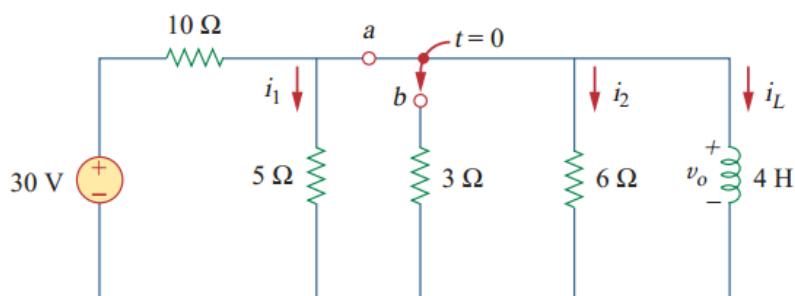
$$V_o(t) = \begin{cases} 0 & t < 0 \\ -20(1 - e^{-12500t}) & 0 < t < 1\text{ms} \\ -10 + 7.65e^{-12500(t-1\text{ms})} & 1\text{ms} < t < \infty \end{cases}$$



- (a) When the switch is in position A, the 5-ohm and 6-ohm resistors are short-circuited so that

$$\underline{i_1(0) = i_2(0) = v_o(0) = 0}$$

but the current through the 4-H inductor is  $i_L(0) = 30/10 = 3\text{ A}$ .

- (b) When the switch is in position B,

$$R_{Th} = 3 // 6 = 2\Omega, \quad \tau = \frac{L}{R_{Th}} = 4/2 = 2\text{ sec}$$


$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)]e^{-t/\tau} = 0 + 3e^{-t/2} = \underline{3e^{-t/2}\text{ A}}$$

$$(c) \quad i_1(\infty) = \frac{30}{10+5} = \underline{2\text{ A}}, \quad i_2(\infty) = -\frac{3}{9}i_L(\infty) = \underline{0\text{ A}}$$

$$v_o(t) = L \frac{di_L}{dt} \longrightarrow \underline{v_o(\infty) = 0\text{ V}}$$


Note that for  $t > 0$ ,  $v_o = (10/15)v_c$ , where  $v_c$  is the voltage across the 25 nF capacitor. Thus we will find  $v_c$  first.

$t < 0$

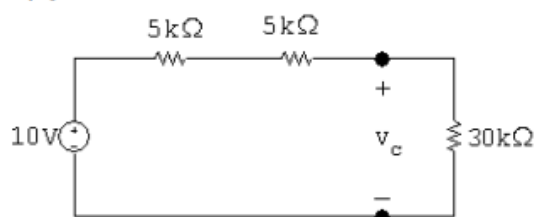

$$v_c(0) = \frac{30}{40}(10) = 7.5 \text{ V}$$

$0 \leq t \leq 0.2 \text{ ms}$ :

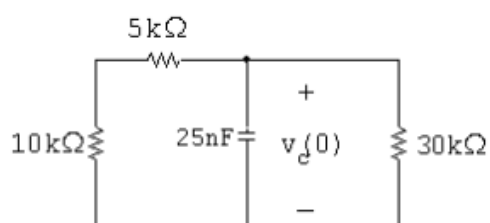


$$\tau = R_e C, \quad R_e = 15,000 \parallel 30,000 = 10 \text{ k}\Omega$$

$$\tau = (10 \times 10^3)(25 \times 10^{-9}) = 0.25 \text{ ms}, \quad \frac{1}{\tau} = 4000$$

$$v_c = 7.5e^{-4000t} \text{ V}, \quad t \geq 0$$

$$v_c(0.2 \text{ ms}) = 7.5e^{-0.8} = 3.37 \text{ V}$$

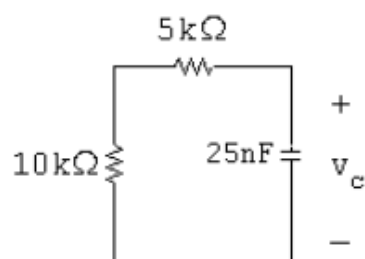
$0.2 \text{ ms} \leq t \leq 0.8 \text{ ms}$ :



$$\tau = (15 \times 10^3)(2.5 \times 10^{-9}) = 375 \mu\text{s}, \quad \frac{1}{\tau} = 2666.67$$

$$v_c = 3.37e^{-2666.67(t-200 \times 10^{-6})} \text{ V}$$

$$0.8 \text{ ms} \leq t <:$$

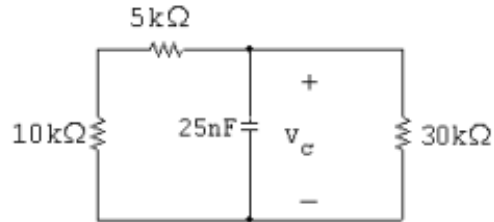

$$\tau = 0.25 \text{ ms}, \quad \frac{1}{\tau} = 4000$$

$$v_c(0.8 \text{ ms}) = 3.37e^{-2666.67(800-200)10^{-6}} = 3.37e^{-1.6} = 0.68 \text{ V}$$

$$v_c = 0.68e^{-4000(t-0.8 \times 10^{-3})} \text{ V}$$


$$v_c(1 \text{ ms}) = 0.68e^{-4000(1-0.8)10^{-3}} = 0.68e^{-0.8} = 0.306 \text{ V}$$

$$v_o = (10/15)(0.306) = 0.204 \text{ V}$$

$$\frac{dv_c}{dt}(0^+) = \frac{1}{C} i_c(0^+)$$

$$\frac{di_L}{dt}(0^+) = \frac{1}{L} V_L(0^+)$$


in  $t = 0^-$

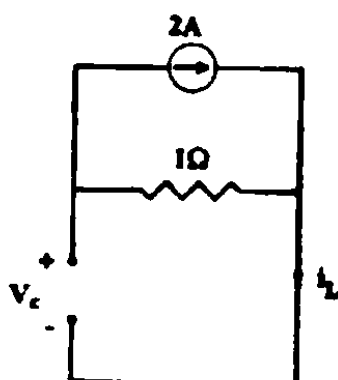

$$i_L(0) = 0$$

$$V_c(0) = -2$$


in  $t = 0^+$

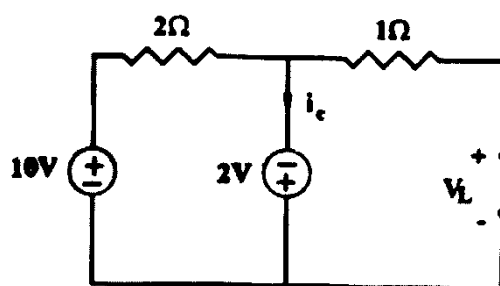

$$\begin{aligned} v_L(0^+) &= -2\text{V} \\ i_c(0^+) &= 6\text{A} \end{aligned} \Rightarrow \begin{cases} \frac{dv_c(0^+)}{dt} = 1 \times 6 = 6 \\ \frac{di_L(0^+)}{dt} = \frac{1}{1} \times -2 = -2 \end{cases}$$

For  $t < 0$ ,  $i(0) = 0$  and  $v(0) = 0$ .

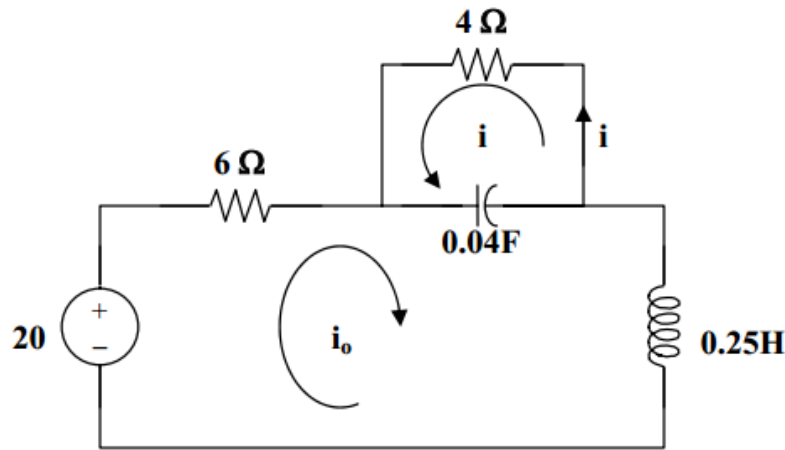For  $t > 0$ , the circuit is as shown below.



Applying KVL to the larger loop,

$$-20 + 6i_o + 0.25di_o/dt + 25 \int (i_o + i)dt = 0 \quad (1)$$

For the smaller loop,  $4i + 25 \int (i + i_o)dt = 0$  or  $\int (i + i_o)dt = -0.16i$  (2)

Taking the derivative,  $4di/dt + 25(i + i_o) = 0$  or  $i_o = -0.16di/dt - i$  (3)

and  $di_o/dt = -0.16d^2i/dt^2 - di/dt$  (4)

From (1), (2), (3), and (4),  $-20 - 0.96di/dt - 6i - 0.04d^2i/dt^2 - 0.25di/dt - 4i = 0$

Which becomes,  $d^2i/dt^2 + 30.25di/dt + 250i = -500$

This leads to,  $s^2 + 30.25s + 250 = 0$

$$\text{or } s_{1,2} = \frac{-30.25 \pm \sqrt{(30.25)^2 - 1000}}{2} = -15.125 \pm j4.608$$



This is clearly an underdamped response.

Thus,  $i(t) = I_s + e^{-15.125t}(A_1\cos(4.608t) + A_2\sin(4.608t))A$ .


At  $t = 0$ ,  $i_o(0) = 0$  and  $i(0) = 0 = I_s + A_1$  or  $A_1 = -I_s$ . As  $t$  approaches infinity,  $i_o(\infty) = 20/10 = 2A = -i(\infty)$  or  $i(\infty) = -2A = I_s$  and  $A_1 = 2$ .

In addition, from (3), we get  $di(0)/dt = -6.25i_o(0) - 6.25i(0) = 0$ .

$di/dt = 0 - 15.125 e^{-15.125t}(A_1\cos(4.608t) + A_2\sin(4.608t)) + e^{-15.125t}(-A_1 4.608\sin(4.608t) + A_2 4.608\cos(4.608t))$ . At  $t=0$ ,  $di(0)/dt = 0 = -15.125A_1 + 4.608A_2 = -30.25 + 4.608A_2$  or  $A_2 = 30.25/4.608 = 6.565$ .

This leads to,
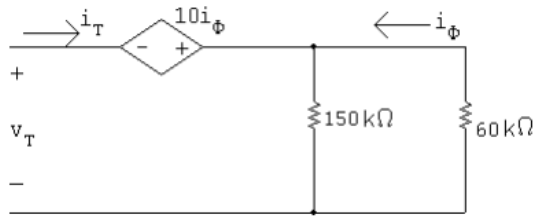
$$i(t) = \underline{(-2 + e^{-15.125t}(2\cos(4.608t) + 6.565\sin(4.608t))) A}$$



$$v_T = -10i_\phi + i_T \left( \frac{(150)(60)}{210} \right) = -10 \frac{-i_T(150)}{210} + i_T \frac{9000}{210}$$

$$\frac{v_T}{i_T} = \frac{1500 + 9000}{210} = 50 \, \Omega$$

$$V_o = \frac{4000}{10,000}(50) = 20 \, \text{V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{20}{50} = -0.4 \, \text{A}$$

$$\frac{i_C(0)}{C} = \frac{-0.4}{8 \times 10^{-6}} = -50,000$$

$$\omega_o = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(51.2 \times 10^{-3})(8 \times 10^{-6})}} = 1562.5 \, \text{rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{(2)(50)(8 \times 10^{-6})} = 1250 \, \text{rad/s}$$

$$\alpha^2 < \omega_0^2 \quad \text{so the response is underdamped}$$

$$\omega_d = \sqrt{1562.5^2 - 1250^2} = 937.5$$


$$v_o = B_1 e^{-1250t} \cos 937.5t + B_2 e^{-1250t} \sin 937.5t$$

$$v_o(0) = B_1 20 \, \text{V}$$

$$\frac{dv_o}{dt}(0) = -\alpha B_1 + \omega_d B_2 = \frac{i_C(0)}{C}$$

$$\therefore \quad -1250(20) + 937.5 B_2 = -50,000 \quad \text{so} \quad B_2 = -26.67$$
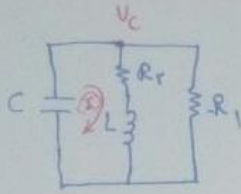
$$v_o = 20e^{-1250t} \cos 937.5t - 26.67e^{-1250t} \sin 937.5t \, \text{V}, \quad t \geq 0$$



$$(KCL) \Rightarrow i_c + i_L + \frac{V_c}{-R_i} = 0$$

$$C \frac{dV_c}{dt} + i_L - \frac{V_c}{R_i} = 0 \quad (1)$$

$$(KVL)_{\text{I}} \Rightarrow V_c = R_r i_L + L \frac{di_L}{dt} \quad (2)$$

$$\text{I, 2} \Rightarrow R_r C \frac{di_L}{dt} + LC \frac{d^2 i_L}{dt^2} + i_L - \frac{R_r}{R_i} i_L - \frac{L}{R_i} \frac{di_L}{dt} = 0$$

$$LC \frac{d^2 i_L}{dt^2} + \left( R_r C - \frac{L}{R_i} \right) \frac{di_L}{dt} + \left( 1 - \frac{R_r}{R_i} \right) i_L = 0$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{LC} \left( R_r C - \frac{L}{R_i} \right) \frac{di_L}{dt} + \frac{1}{LC} \left( 1 - \frac{R_r}{R_i} \right) i_L = 0$$

$$\left\{ \begin{array}{l} \gamma_d = 0 \\ \omega_d^2 > 0 \end{array} \right.$$

شماره های زوج

$$\gamma_d = \frac{1}{LC} \left( R_r C - \frac{L}{R_i} \right) = 0$$

$$R_i = \frac{L}{R_r C}$$

$$\omega_d^2 = \frac{1}{LC} \left( 1 - \frac{R_r}{R_i} \right) > 0$$

$$R_i > R_r$$