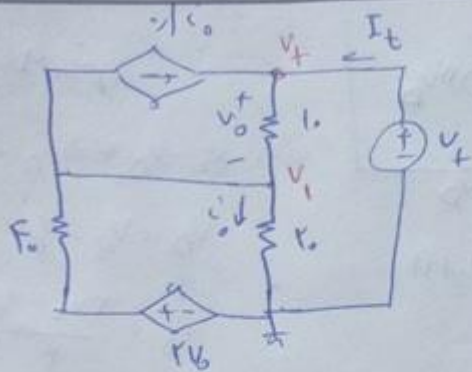


جواب سوالات 3 Homework 3

-۲



$$(k(1))_{V_t} \Rightarrow \frac{V_t - V_1}{r_0} = I_t - \beta i_0 \quad , \quad i_0 = \frac{V_1}{r_0}$$

$$\frac{V_t - V_1}{r_0} = I_t - \beta \frac{V_1}{r_0}$$

$$r_0 V_t - r_0 V_1 = r_0 I_t - \beta V_1 \quad , \quad V_1 = \frac{r_0 V_t - r_0 I_t}{r_1} \quad (1)$$



$$(k(1))_{V_1} \Rightarrow \frac{V_1}{r_0} + \frac{V_1 - V_t}{r_0} + \beta i_0 + \frac{V_1 - r_0 V_t}{r_0} = 0 \quad , \quad V_0 = V_t - V_1$$

$$\frac{V_1}{r_0} + \frac{V_1 - V_t}{r_0} + \frac{V_1}{r_0} + \frac{\beta V_1 - \beta r_0 V_t}{r_0} = 0 \quad , \quad V_1 = \frac{r_0}{r_1} V_t \quad (2)$$

$$(1,2) \Rightarrow \frac{r_0 V_t - r_0 I_t}{r_1} = \frac{r_0}{r_1} V_t$$


$$r_0 V_t - r_0 I_t = r_0 V_t$$
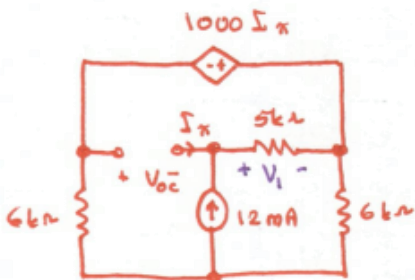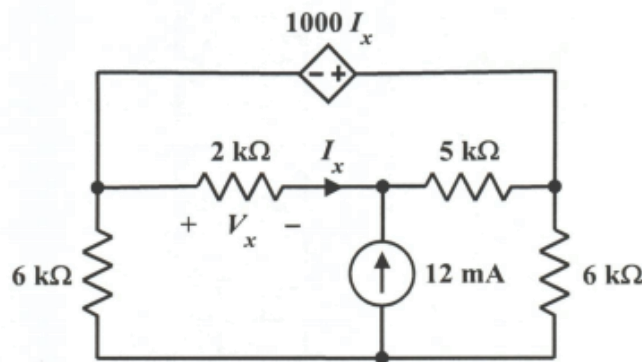
$$V_t = \underbrace{r_1}_{R_{th}} I_t + \underbrace{0}_{V_{th}}$$



$$I_x = 0 \Rightarrow V_1 = (5k\Omega)(12mA) = 60V$$
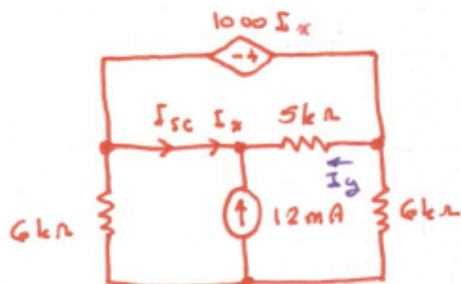
$$\Rightarrow 1000 I_x = 0 \Rightarrow V_{OC} = -V_1 = -60V$$



$$I_y = \frac{1000 I_x}{5k\Omega} = \frac{1}{5} I_x$$


$$I_y + I_x = -12mA \Rightarrow 1.2 I_x = -12mA$$

$$\therefore I_x = -10mA$$

$$I_{SC} = I_x = -10mA$$

$$V_T = V_{OC} = -60V$$

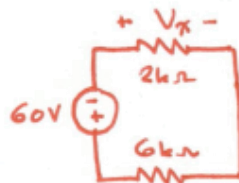
$$R_T = \frac{V_{OC}}{I_{SC}} = \frac{-60V}{-10mA} = 6k\Omega$$



$$V_x = - \frac{2k\Omega}{2k\Omega + 6k\Omega} (60V) = -15V$$

[a] First find the Thévenin equivalent with respect to R_o .

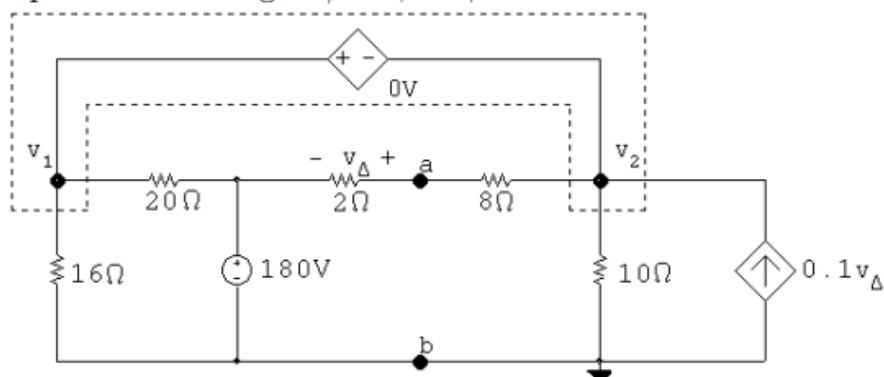Open circuit voltage: $i_\phi = 0$; $184\phi = 0$




$$\frac{v_1}{16} + \frac{v_1 - 180}{20} + \frac{v_1 - 180}{10} + \frac{v_1}{10} - 0.1v_\Delta = 0$$

$$v_\Delta = \frac{v_1 - 180}{10}(2) = 0.2v_1 - 36$$

$$v_1 = 80 \text{ V}; \quad v_\Delta = -20 \text{ V}$$

$$V_{\text{Th}} = 180 + v_\Delta = 180 - 20 = 160 \text{ V}$$

Short circuit current

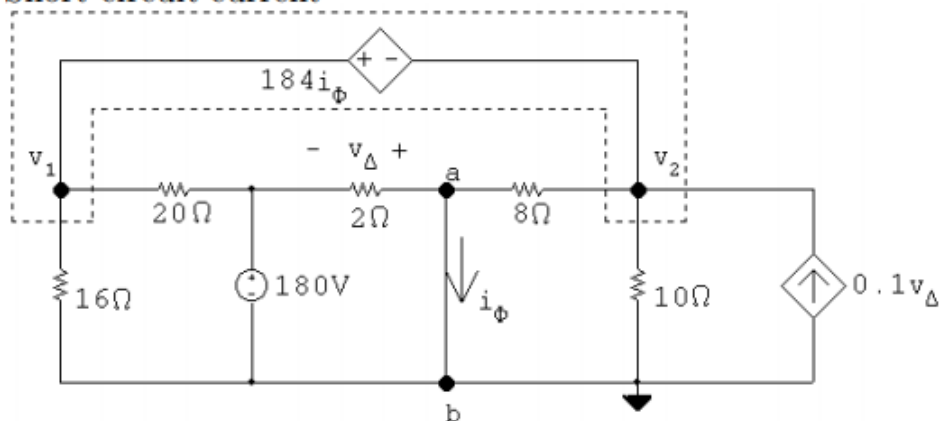

$$\frac{v_1}{16} + \frac{v_1 - 180}{20} + \frac{v_2}{8} + \frac{v_2}{10} - 0.1(-180) = 0$$

$$v_2 + 184i_\phi = v_1$$

$$i_\phi = \frac{180}{2} + \frac{v_2}{8} = 90 + 0.125v_2$$


$$v_2 = -640 \text{ V}; \quad v_1 = 1200 \text{ V}$$

$$i_{\phi} = i_{sc} = 10 \text{ A}$$

$$R_{Th} = V_{Th}/i_{sc} = 160/10 = 16 \Omega$$


$$\therefore R_o = 16 \Omega$$

[b]

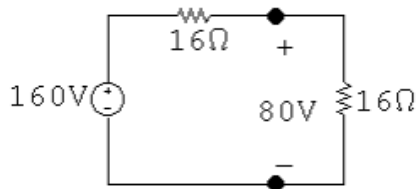

$$p_{\max} = (80)^2/16 = 400 \text{ W}$$

[c]

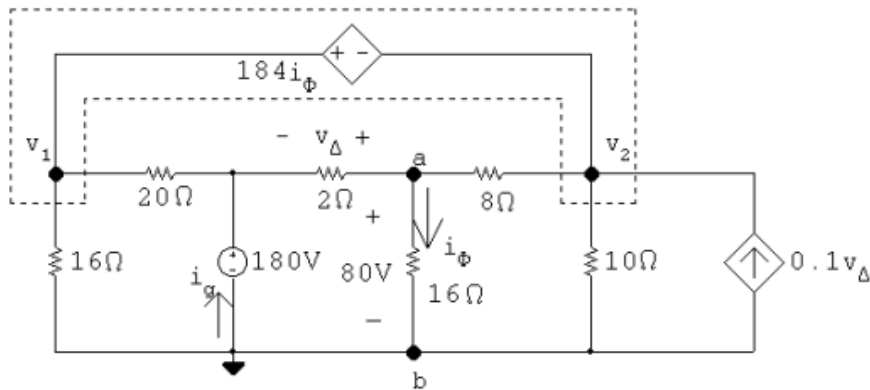

$$\frac{v_1}{16} + \frac{v_1 - 180}{20} + \frac{v_2 - 80}{8} + \frac{v_2}{10} - 0.1(80 - 180) = 0$$

$$v_2 + 184i_{\phi} = v_1; \quad i_{\phi} = 80/16 = 5 \text{ A}$$


Therefore, $v_1 = 640 \text{ V}$ and $v_2 = -280 \text{ V}$; thus,

$$i_g = \frac{180 - 80}{2} + \frac{180 - 640}{20} = 27 \text{ A}$$


$$p_{180\text{V}} (\text{dev}) = (180)(27) = 4860 \text{ W}$$

$$400 \cdot 100 / 4860 = 8.23 \%$$

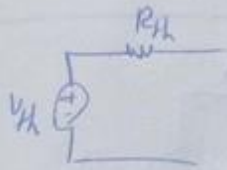
الف) فرض کنید معادل تئری مدار به صورت مقابل باشد:



الف)

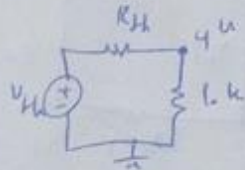

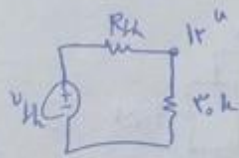
$$4 \mu = \frac{10k}{R_{th} + 10k} \times V_{th} \Rightarrow 40 + 4R_{th} = 10V_{th} \quad (1)$$



$$12 \mu = \frac{30k}{30k + R_{th}} \times V_{th} \Rightarrow 360 + 12R_{th} = 30V_{th} \quad (2)$$

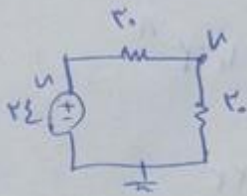
1, 2) $\Rightarrow V_{th} = 24 \mu$, $R_{th} = 30k \Omega$



ب)

$$u = \frac{30}{30 + 30} \times 24 = 9,4 \mu$$

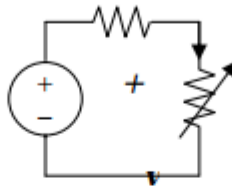We replace the box with the Thevenin equivalent.



$$V_{Th} = v + iR_{Th}$$

When $i = 1.5$, $v = 3$, which implies that $V_{Th} = 3 + 1.5R_{Th}$ (1)


When $i = 1$, $v = 8$, which implies that $V_{Th} = 8 + 1R_{Th}$ (2)

From (1) and (2), $R_{Th} = 10$ ohms and $V_{Th} = 18$ V.


(a) When $R = 4$, $i = V_{Th}/(R + R_{Th}) = 18/(4 + 10) = \underline{\underline{1.2857 \text{ A}}}$

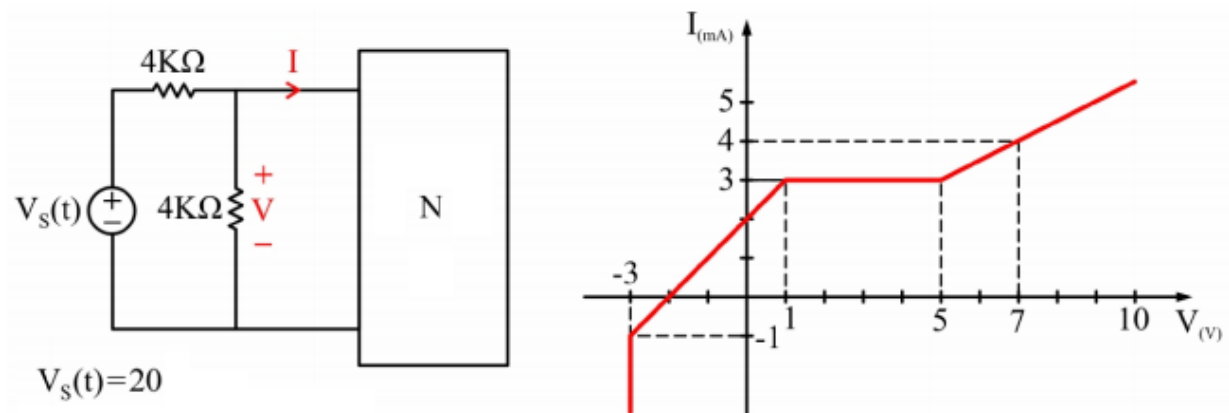(b) For maximum power, $R = R_{Th}$

$$P_{max} = (V_{Th})^2/4R_{Th} = 18^2/(4 \times 10) = \underline{\underline{8.1 \text{ watts}}}$$



First find the Thévenin equivalent

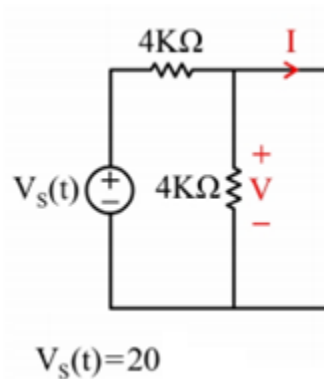


$$R_{th} = 2K\Omega, \quad e_{oc} = \frac{V_s}{2} \Rightarrow V = 2I + \frac{V_s}{2}$$

The relationship between voltage and current for the above figure is obtained as follows

$$V = -2I + 10$$

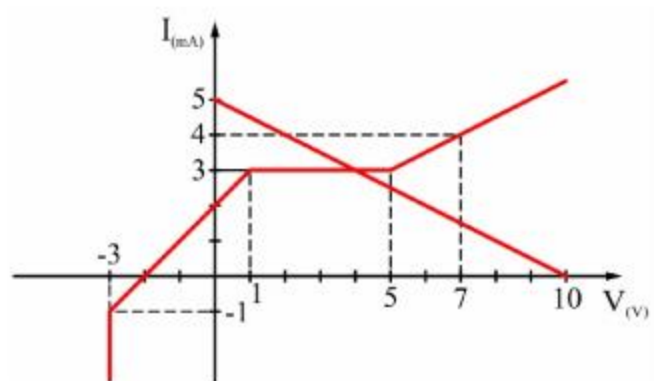Then we obtain the intersection point of this equation with the V-I diagram of bipolar N:



$$\Rightarrow i=3 \Rightarrow V = -2 \times 3 + 10 = 4$$